

Date: 07.10.2019

Time : (3 Hours)

Total Marks: 100

- N.B. (1) All questions are compulsory.
 (2) Figures to the right indicate marks for respective sub questions.
 (3) Use of **Non-programmable** calculators is **allowed**.
 (4) Draw **neat labeled diagrams** wherever **necessary**.
 (5) Symbols used have their usual meaning

Q.1) [A] Choose correct alternative in each of the following. (12)

- (i) Volume element in Cylindrical coordinate system is given as ---
 (a) $r^2 dr d\theta dz$ (b) $r^2 \sin \theta dr d\theta dz$
 (c) $r^2 dr d\theta d\phi$ (d) $r dr d\theta dz$
- (ii) A necessary and sufficient condition that line integral $\int \vec{A} \cdot d\vec{r} = 0$ for every closed curve is
 (a) $\text{Div } \vec{A} = 0$ (b) $\text{Div } \vec{A} \neq 0$
 (c) $\text{Curl } \vec{A} \neq 0$ (d) $\text{Curl } \vec{A} = 0$
- (iii) Operating point represents _____.
 (a) Zero signal values of I_C & V_{CE} (b) high signal values of I_C & V_{CE}
 (c) low signal values of I_C & V_{CE} (d) Current factor
- (iv) A CE-amplifier produces _____.
 (a) Phase reversal (b) Shift divider
 (c) Maximum reversal (d) Minimum reversal
- (v) An electronic oscillator is an amplifier with _____ feedback.
 (a) Negative (b) Positive & negative
 (c) positive (d) zero
- (vi) An ideal Op-amp has _____ offset voltage.
 (a) Zero input (b) Low level
 (c) Zero output (d) Infinite output

[B] Answer in One Sentence (3)

- (i) What is current gain?
 (ii) What are coordinates of spherical coordinate system?
 (iii) State any one condition to get sustained oscillations.

[C] Fill in the blanks (5)

- (i) The input resistance of an ideal op-amp is -----.
 (ii) Divergence theorem states that $\int (\vec{\nabla} \cdot \vec{A}) dv$ is equal to the _____ integral of \vec{A} over closed surface.
 (iii) If $\phi(x, y, z)$ is a single valued then line integral between two points is path -----
 -----.
 (iv) An oscillator circuit must satisfy _____.
 (v) Faithful amplification is the process of raising the strength of a weak signal without any change in its _____.

Q.2) [A] Attempt **any ONE** of the following. (8)

- (i) Check the fundamental theorem for Gradient, using $T = x^2 + 4xy + 2yz^3$ the points $A=(0,0,0), B = (1,1,1)$ and the three path are as follows
- $(0,0,0) \rightarrow (1,0,0) \rightarrow (1,1,0) \rightarrow (1,1,1)$
 - $(0,0,0) \rightarrow (0,0,1) \rightarrow (0,1,1) \rightarrow (1,1,1)$
 - The parabolic path $z = x^2, y = x$
- (ii) Let $\vec{A} = (2xz + 3y^2)\hat{y} + 4yz^2\hat{z}$ check fundamental theorem for curl for plane square surface in YZ – plane such that $Y=Z=1$ and $x = 0$.

[B] Attempt **any ONE** of the following. (8)

- (i) State and explain the fundamental theorem of Divergence. Check the Divergence theorem using vector function $\vec{A} = xy\hat{i} + 2yz\hat{j} + 3xz\hat{k}$. Consider a cube of side of length two units and having vertex at origin.
- (ii) What is surface integral? Calculate the close surface integral for $\vec{A} = 4xz\hat{i} - y^2\hat{j} + yz\hat{k}$ Consider a cube of side of length two units and having vertex at origine.

[C] Attempt **any ONE** of the following. (4)

- (i) Calculate surface area and Volume of sphere having radius R in spherical coordinate system.
- (ii) Find the expression for length and surface element in cylindrical coordinate system.

Q.3) [A] Attempt **any ONE** of the following. (8)

- (i) Draw the circuit diagram of CE amplifier using voltage divider method for transistor biasing. Show that the stability factor is unity. Give one advantage and disadvantage of this method.
- (ii) What are the advantages of negative feedback in an amplifier? State the influence of negative feedback on the various amplifier parameters.

[B] Attempt **any ONE** of the following. (8)

- (i) Draw the circuit diagram of CE amplifier using Base Resistor method for transistor biasing. Deduce the equation for stability factor. Give advantages and disadvantages of this method.
- (ii) Derive a general expression for gain of the amplifier with feedback. What is loop gain?

[C] Attempt **any ONE** of the following. (4)

- (i) An amplifier has an input signal voltage 0.1 volt and draws 0.1mA from the source. The amplifier delivers 5 volts to a load at 10mA. Determine the voltage gain, current gain and power gain.
- (ii) In base resistor method, if $V_{CC} = 12 \text{ V}$, $R_B = 300 \text{ K}\Omega$, $R_C = 2\text{K}\Omega$, $\beta = 100$ is used then find V_C . Neglect V_{BE} .

- Q.4) [A] Attempt **any ONE** of the following. (8)
- (i) Draw the circuit diagram and explain the working of Colpitt's oscillator. Write the expression for feedback fraction and frequency of oscillations.
 - (ii) What do you mean by inverting amplifier? Draw the circuit diagram of Inverting amplifier using op-amp. Derive the expression for gain of the circuit.
- [B] Attempt **any ONE** of the following. (8)
- (i) With the help of neat labelled diagram explain the circuit operation of Wien Bridge oscillator. Obtain the expression for frequency of oscillations.
 - (ii) Explain in the action of an Op-amp as an Integrator and Differentiator.
- [C] Attempt **any ONE** of the following. (4)
- (i) A Colpitt's oscillator has $L = 1 \text{ mH}$, $C_1 = 1000 \text{ pF}$ and $C_2 = 5000 \text{ pF}$. Find the frequency of oscillation.
 - (ii) In the non-inverting amplifier circuit, $R_1 = 1 \text{ k}\Omega$, $R_f = 10 \text{ k}\Omega$. If the input to the non-inverting terminal is 0.2 V , what is the output voltage? If the output saturation voltage is 11 volt , what is the maximum possible input voltage for linear operation?
- Q.5) Attempt **any FOUR** of the following. (20)
- (i) Explain the basic concept of amplification.
 - (ii) Write essential of a transistor biasing circuit.
 - (iii) Calculate the volume integral for $v = 4z - y$ by considering volume element as cube with sides of length two units and having one vertex at origin.
 - (iv) Calculate the work done when a force $\vec{F} = 2xy\hat{i} - 3y^2\hat{j}$ moves a particle in the xy-plane from origin to a point P(1,2) along the parabola $y = x^2$.
 - (v) Draw block diagram of oscillator. What are the requirements of sustained oscillations?
 - (vi) Write any Five ideal characteristics of an ideal op-amp.
-